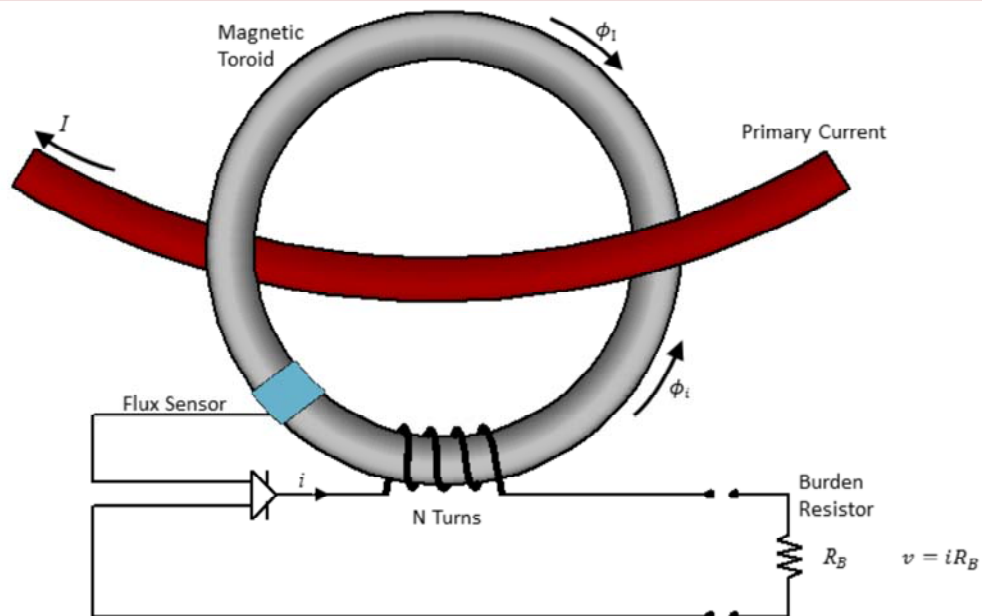


Zero Flux Current Transducer, Principle




Principle of Zero Flux Current Transducer

GMWAssociates

1

The primary current, I , in a conductor through a magnetic core will generate a magnetic flux in the core ϕ_I . If somehow this flux in the core can be sensed by a "core flux sensor" then a compensation current, i , in a winding around the core can be used to generate an opposite flux ϕ_i so that $\phi_i = \phi_I$. The compensation current, I , can be measured in a "Burden Resistor" R_B as $v = I \cdot R_B$.


Zero Flux Current Transducer, Principle

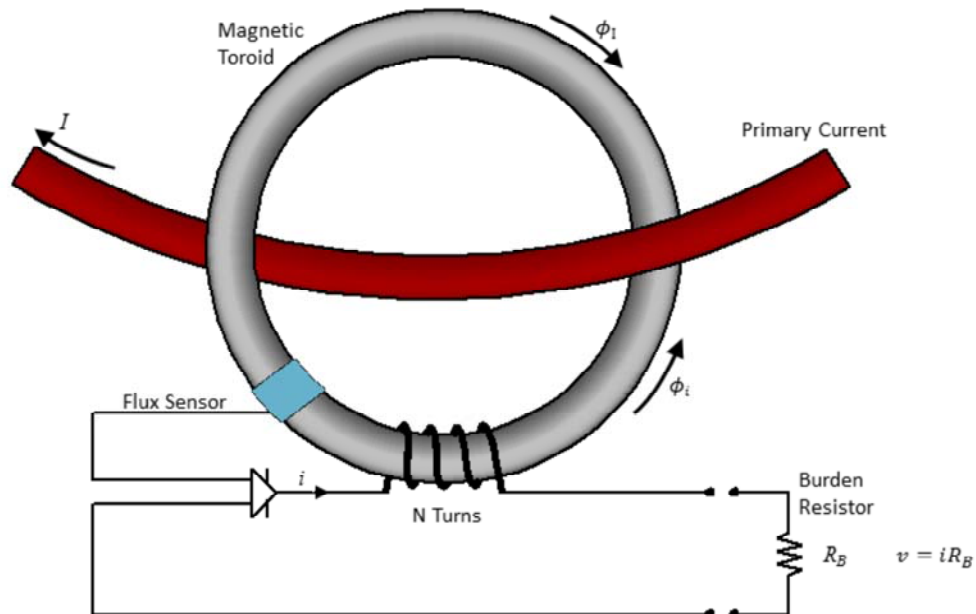

If $\phi_2 = \phi_1$ (zero flux in the magnetic toroid), $Ni = I$ and $i = I/N$ ($N \sim 200$ to 5000).

With this arrangement the basic requirements of a Current Transducer have been achieved. The output current, i , is reduced from the primary current, I , to $\frac{I}{N}$ where N is a fixed constant, the number of turns in the compensation winding. Also the output current, i , is electrically isolated from the primary current, I .

Zero Flux Current Transducer, Principle

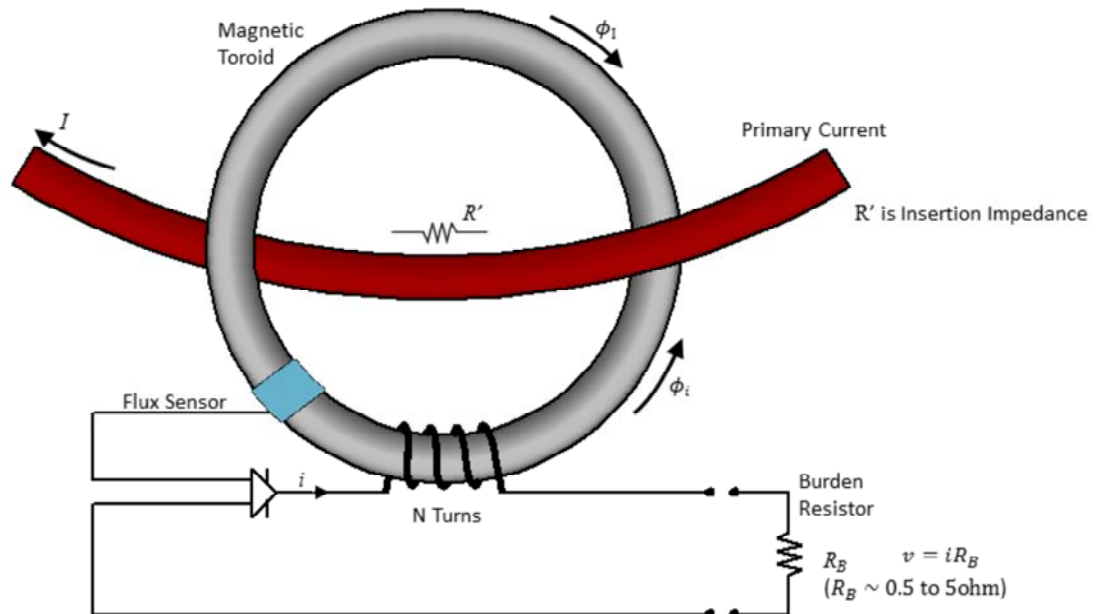

If $\phi_i = \phi_1$ (zero flux in the magnetic toroid), $Ni = I$ and $i = I/N$ ($N \sim 200$ to 5000).

If there is no power lost in the Current Transducer, $I^2 R' \sim i^2 R_B$, $I^2 R' \sim \frac{I^2}{N^2} R_B$ or $R' \sim \frac{R_B}{N^2}$

For $R_B \sim 1\text{ohm}$, $N \sim 1000$, $R' \sim 1\mu\text{ohm}$. For $I \sim 1000\text{A}$, $N \sim 1000$, Power $\sim 1\text{W}$

Principle of Zero Flux Current Transducer

GMW Associates

3

If there is no power lost in the toroid and the compensation winding, then the equivalent insertion impedance, R' , of the Current Transducer can be estimated by equating the power dissipated in R' with the power dissipated in the Burden Resistor R_B . This shows that the equivalent insertion impedance is the Burden Resistance R_B/N^2 .

Not only does the Current Transducer provide electrical isolation and current division but also a dramatic reduction in the insertion loss compared to using a low resistance shunt to measure the primary current.

The typical insertion impedance can be about $1\mu\text{ohm}$ with a peak series power dissipation in the primary circuit of about 1W at 1000A .